

USN

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

**RV COLLEGE OF ENGINEERING®**  
 (An Autonomous Institution affiliated to VTU)  
**III Semester B. E. Examinations April/May - 2023**  
**Computer Science and Engineering**  
**LOGIC DESIGN**

*Time: 03 Hours**Maximum Marks: 100**Instructions to candidates:*

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

**PART-A**

|   |      |   |    |
|---|------|---|----|
| 1 | 1.1  | What are state diagrams and state tables?   | 02 |
|   | 1.2  | 16:1 multiplexer circuit will have _____ select lines.  | 01 |
|   | 1.3  | The minterm designator for the term $\overline{A}BC\overline{D}$ is _____.  | 01 |
|   | 1.4  | A n-stage Johnson counter has _____ states.   | 01 |
|   | 1.5  | _____ is an IC with programmable gates divided into an AND array and an OR array to provide an AND – OR – SOP implementation. | 01 |
|   | 1.6  | The flip-flop that follows the input is a _____ flip-flop.  | 01 |
|   | 1.7  | Draw the logical diagram of a 1bit magnitude comparator.  | 02 |
|   | 1.8  | Define a register.  | 01 |
|   | 1.9  | A counter with 4 flip-flops will have _____ unique states.  | 01 |
|   | 1.10 | Write the truth table and block diagram of 2:4 line decoder.  | 02 |
|   | 1.11 | Draw the timing diagram of a 2 bit down counter with negative edge triggered flip-flops.                                      | 02 |
|   | 1.12 | What is the supply voltage level of TTL IC's?   | 01 |
|   | 1.13 | Simplify the Boolean expression: $Y = \overline{(A + B + C)} + (B + \overline{C})$  | 02 |
|   | 1.14 | How many JK flip-flops are required to achieve the frequency division of 8?   | 01 |
|   | 1.15 | A device which converts BCD to seven segment is called _____.   | 01 |

**PART-B**

|   |   |   |    |
|---|---|---|----|
| 2 | a | Minimize the following Boolean expression using K map:<br>i) $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$<br>ii) $F(A, B, C, D) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \sum d(0, 2, 14)$ | 08 |
|   | b | Simplify the following Boolean function $f(w, x, y, z) = \sum(0, 2, 5, 7, 10, 13, 14, 15)$ using Quine-McCluskey tabular method.  | 08 |
| 3 | a | With a neat diagram, explain a decimal adder.   | 08 |
|   | b | Implement the Boolean function using 8:1 and also using 4:1 multiplexer $F(A, B, C, D) = \sum M(0, 2, 4, 6, 9, 12, 14)$ .   | 08 |

