

USN

--	--	--	--	--	--	--	--	--	--

RV COLLEGE OF ENGINEERING®
(An Autonomous Institution affiliated to VTU)
III Semester B. E. Fast Track Examinations Oct-2020
Computer Science and Engineering
LOGIC DESIGN

*Time: 03 Hours**Maximum Marks: 100***Instructions to candidates:**

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2, 7 and 8 are compulsory. Answer any one full question from 3 and 4 & one full question from 5 and 6

PART-A

1	1.1	Realize the logic circuit for the Boolean equation $Y = A + B$ using <i>NAND</i> gates.	02
	1.2	Construct the karnaugh map for the Boolean expression function $F(A, B, C, D) = \sum m(7) + d(10, 11, 12, 13, 14, 15)$.	02
	1.3	Distinguish between static and dynamic hazards in logic devices.	02
	1.4	What is the maximum number of inputs for an <i>OR</i> gate in a 4-bit parallel adder?	01
	1.5	Perform 2's complement subtraction between -43 and -78 .	02
	1.6	Show the clocked <i>RS</i> flip flop using only <i>NAND</i> gates.	02
	1.7	Write any two differences between encoders and decoders.	02
	1.8	Distinguish between an edge-triggered and pulse triggered <i>JK</i> flip flop.	02
	1.9	Draw a logic circuit for positive-edge triggered <i>JK</i> flip flop.	02
	1.10	What is Ring counter?	01
	1.11	What modulus counter can be constructed with the use of five flip flops?	01
	1.12	Write the state sequence of a modulo-6 counter.	01

PART-B

2	a	Design a Karnaugh map for the Boolean equation expressed by minterms: $Y = F(A, B, C, D) = \sum m(7, 9, 10, 11, 12, 13, 14, 15)$ Also write the simplified Boolean expression along with the corresponding logic circuit.	08
	b	Find all the prime implicants of the function $f(a, b, c) = \sum (0, 1, 2, 5, 6, 7)$. Also design a logic circuit for the realized expression.	08
3	a	Using binary adder subtract logic block diagram, illustrate the working of 8 bit binary adder with an example.	08
	b	Design a 32 to 1 multiplexer using two 16-1 multiplexers and one 2 to 1 multiplexer. Illustrate the working operation of the logic circuit.	08
OR			

4	a	Create a logic circuit to show multi input <i>OR</i> gates using a 3 to 8 decoder for the Boolean expression : $F1(A,B,C) = \sum m(0,4,6)$ $F2(A,B,C) = \sum m(0,5), F2(A,B,C) = \sum m(1,2,3,7)$	08
	b	With the help of a block diagram, truth table, analyze the working of two 1-bit comparator.	08
5	a	Draw the <i>JK</i> master-slave flip flop block diagram and briefly explain the operation with corresponding waveform and truth table.	08
	b	What is characteristic equation of a flip flop? Analyze the characteristic equations of <i>SR</i> and <i>T</i> -flip flop along with its truth table.	08
OR			
6	a	Draw the waveforms to shift the numbers 0100 using 4-bit serial input shift register. Also explain its operation with the help of logic block diagram.	08
	b	Show how modulo-8 switched tail counter works if it is initialized with 1001. How to decode this counter?	08
7	a	Draw the logic diagram and waveforms for three-bit binary ripple counter. Also illustrate its working operation in detail along with the truth table.	10
	b	What are the differences between synchronous and asynchronous counters? Mention any two real-time applications of it.	06
8	a	What are the differences between Moore and Melay model. Using state transition diagram briefly explain each one in detail.	08
	b	Analyze the Melay model asynchronous sequential circuit shown in fig 8b and show its stable state and corresponding outputs. Give the state diagram of this circuit.	08

 


Fig 8b